

Digital to Analog Converters

2/20/2004


Costas Foudas, Imperial College,
Rm: 508, x47590

1



Recall: The 741 Op.Amp IV

Summing Amplifier :

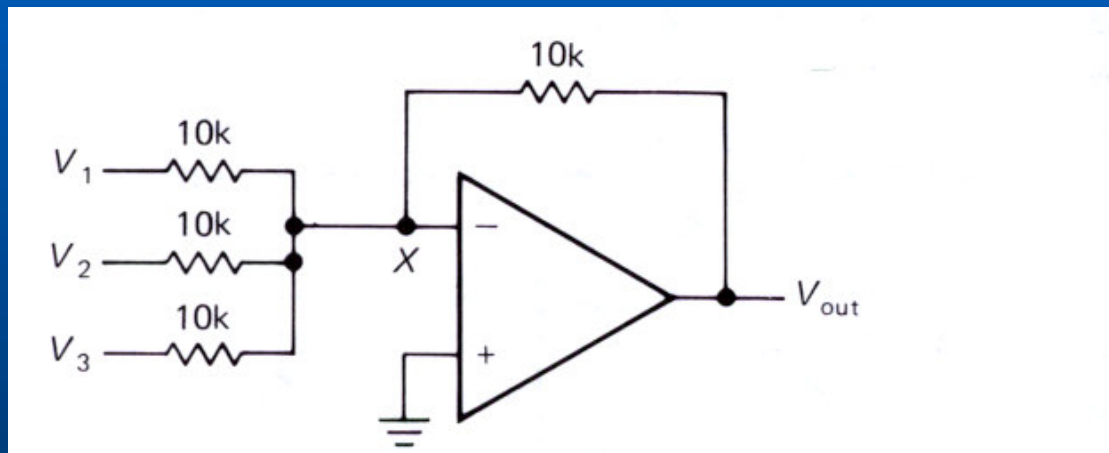


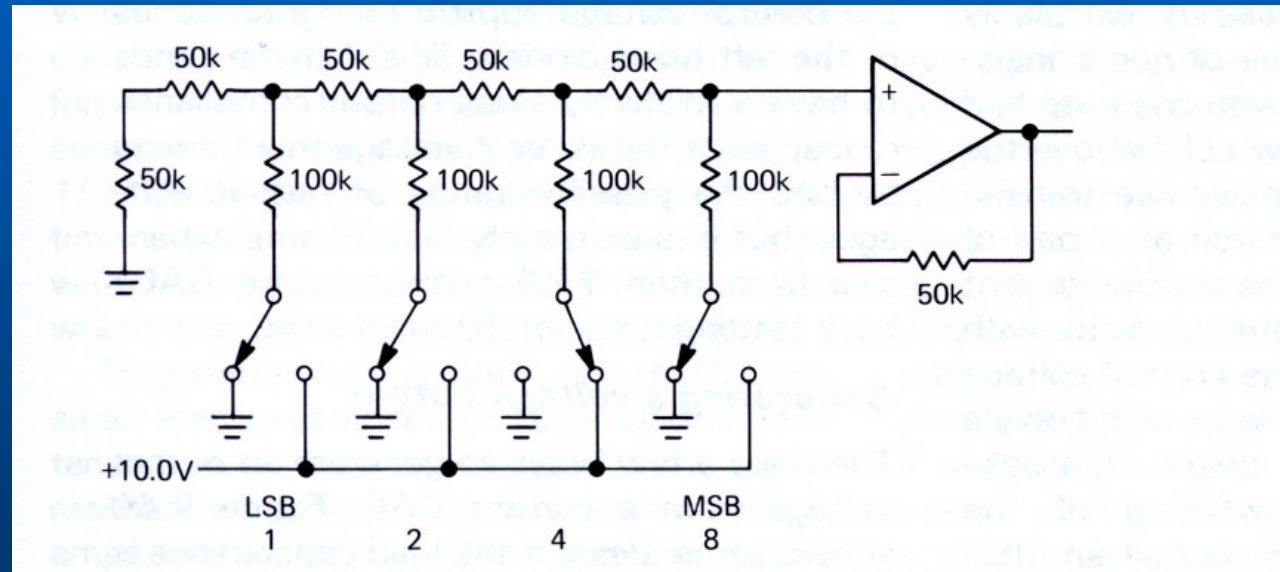Exercise : Show that $V_{out} = - (V1+V2+V3)$



The 741 Op.Amp IV

R-2R Network to convert digital to analog




**By now you should know how does
It work...**



Operation I


The **DIGITAL** to **ANALOG CONVERTERS** (DAC) are devices that convert digital to analog signals:

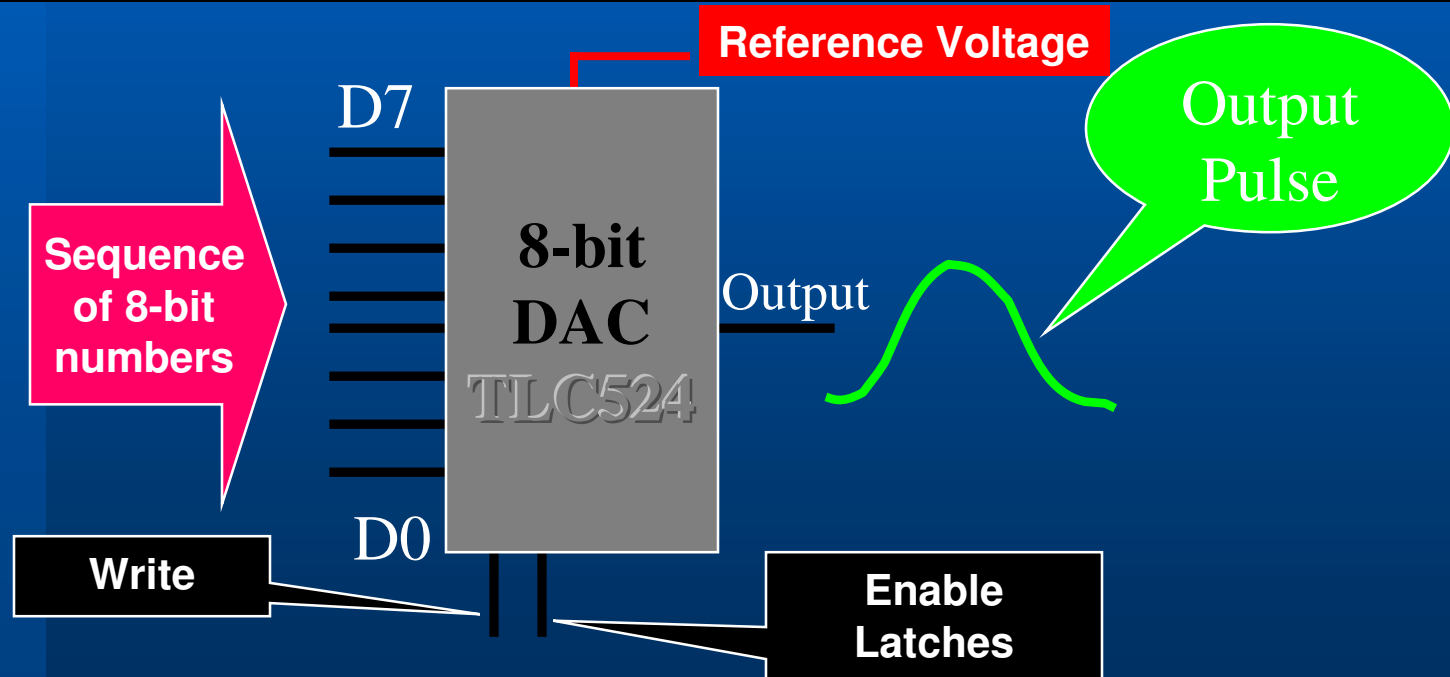



Operation II

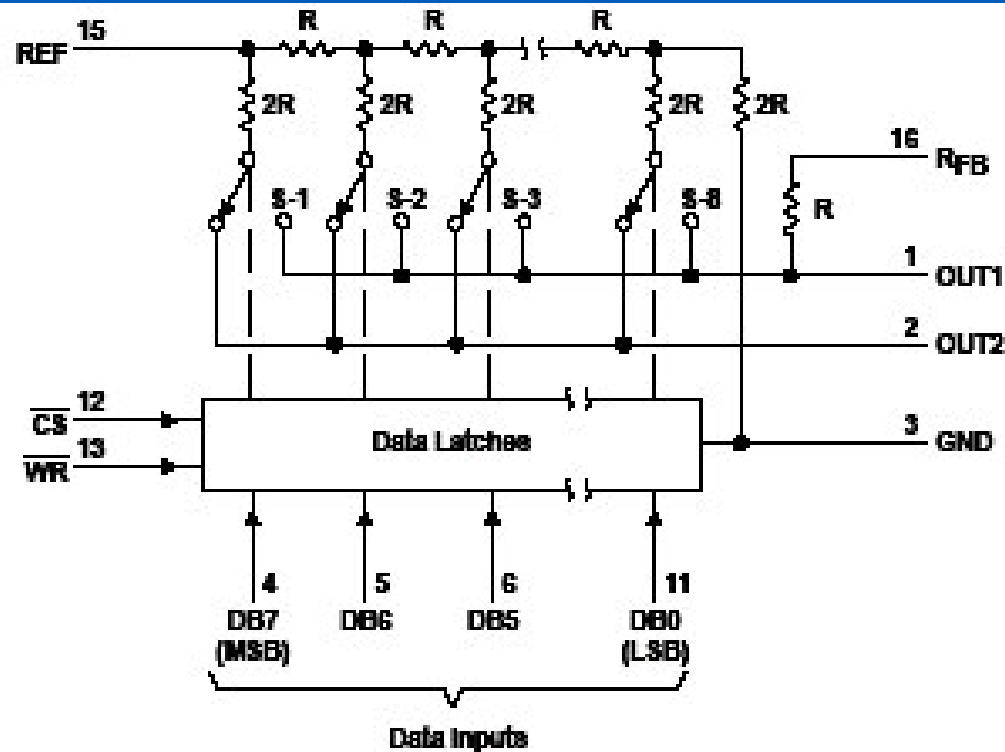The basic operational idea of the DAC we will be using is:




Terminal numbers shown are for the D or N package.



Write Cycles of the TLC7524

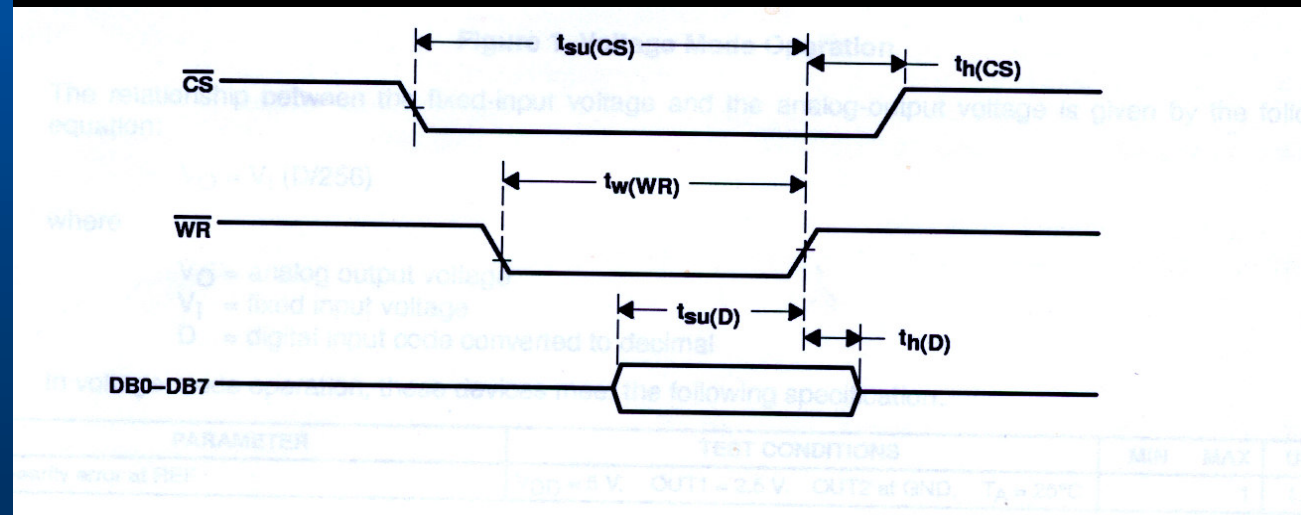The DAC has internal registers to store the data (1 Byte) and signals which control the write operation (**CS***, **WR***):





The TLC7524 DAC

For your analog signal generator you will be using an 8-bit DAC to convert the 8-bit Signals, from the ATmega103 ports, to analog Signals of given frequency, amplitude and offset.

16 15 14 13 12 11 10 9



1 2 3 4 5 6 7 8



The TLC7524 Data Sheet


Recommended operating conditions :

	V _{DD} = 5 V			V _{DD} = 15 V			UNIT
	MIN	NOM	MAX	MIN	NOM	MAX	
Supply voltage, V _{DD}	4.75	5	5.25	14.5	15	15.5	V
Reference voltage, V _{ref}	±10			±10			V
High-level input voltage, V _{IH}	2.4	2.5		13.5	14	15	V
Low-level input voltage, V _{IL}		1.0	0.8		10	1.5	V
CS setup time, t _{su} (CS)	40			40			ns
CS hold time, t _h (CS)	0			0			ns
Data bus input setup time, t _{su} (D)	25			25			ns
Data bus input hold time, t _h (D)	10			10			ns
Pulse duration, $\overline{\text{WR}}$ low, t _w (WR)	40			40			ns
Operating free-air temperature, T _A	TLC7524C			0		70	°C
	TLC7524I			-25		85	
	TLC7524E			-40		85	



Producing a Voltage Level

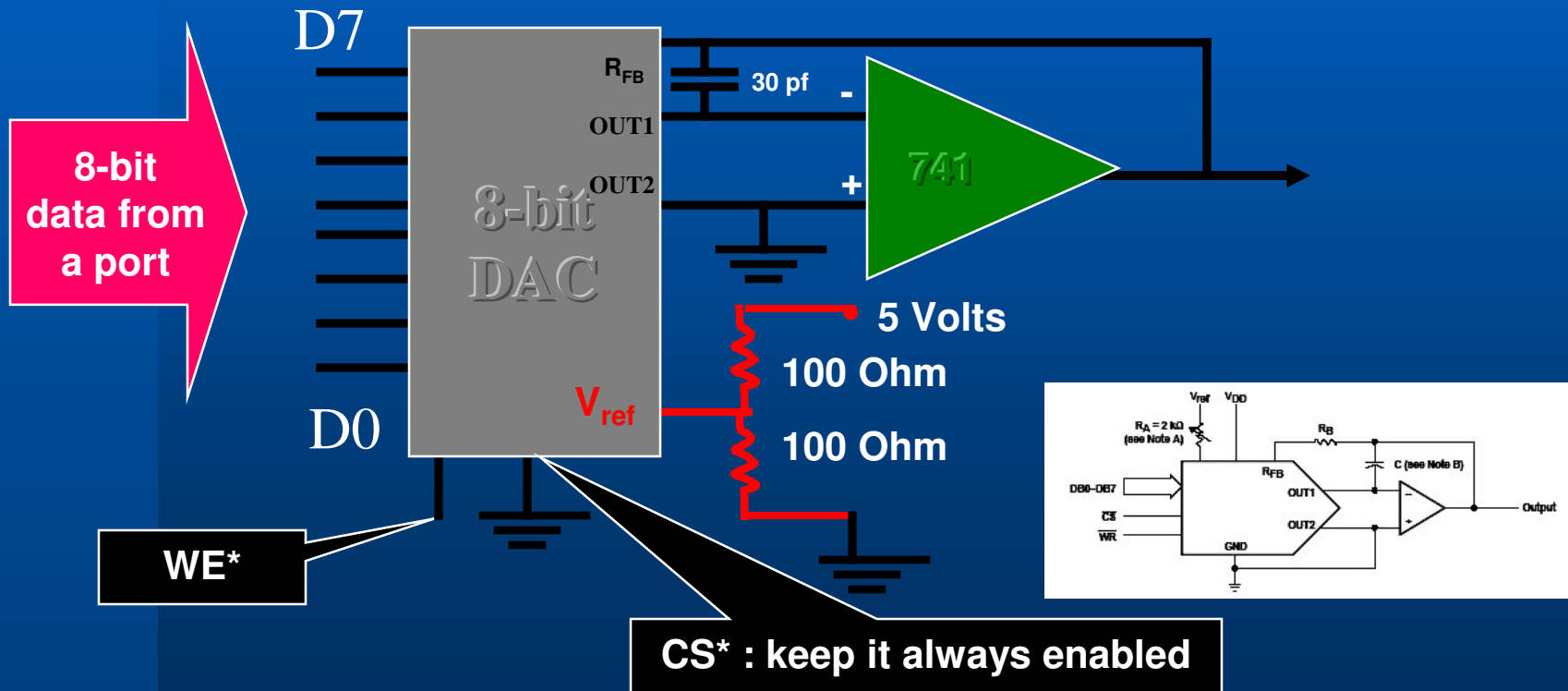You can write numbers to the DAC in a similar way as with the 3-byte memory module using the ATmega103 Ports





Task Plan

Design and construct a Signal Generator:

- The ATmega103 should be used to design a signal generator. The Amplitude, Frequency and Voltage offset should be subject to change under program control.
- The signals should be produced using a DAC and an Operational Amplifier driven by one of the ATmega103 ports.
- The generator should have a user interface.
- The LCD should be used to display a menu and the given frequency amplitude and offset settings.
- The Keyboard should be used for user input.