

Passive Filters

2/19/2004

Costas Foudas, Imperial College,
Rm: 508, x47590


1



Review: RLC in Series

$$(1) V_L = L \, di/dt$$

$$(2) V_C = 1/C \int i \, dt$$

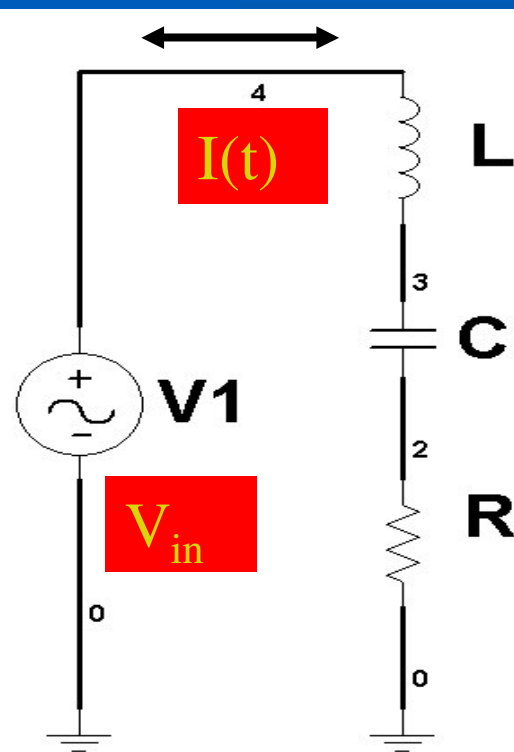

Suppose that: $I(t) = I_{ph} e^{i\omega t}$;

$V_{in} = V(t)$ such that $Z = V_{in}/I(t)$

$$I Z = I R + 1/c \int I dt + L di/dt \Rightarrow$$

$$I Z = I R + 1/(i \omega c) I + (i \omega L) I \Rightarrow$$

$$Z = R - i/(\omega c) + (i \omega L)$$


$$Z_R = R$$

$$Z_C = -i/(\omega c)$$

$$Z_L = i(\omega L)$$



Review: RLC in Parallel

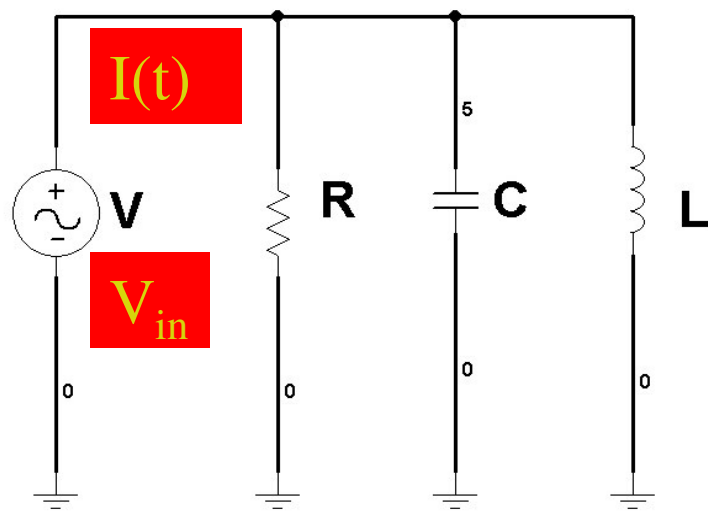

$$(1) I_C = C \, dV/dt$$

$$(2) I_L = 1/L \int V dt$$

Suppose that: $V(t) = V_{ph} e^{i\omega t}$;

$I = I(t)$ such that $Z = V_{in}/I(t)$

$$I = V_{in}/Z = V_{in}/R + 1/L \int V dt + C \, dV/dt \Rightarrow$$


$$V_{in}/Z = V_{in}/R + 1/(i \omega L) V_{in} + (i \omega C) V_{in} \Rightarrow$$

$$1/Z = 1/R + 1/(-i/\omega C) + 1/(i \omega L)$$

$$Z_R = R \quad Z_C = -i/(\omega C) \quad Z_L = i(\omega L)$$



High Pass Filter I

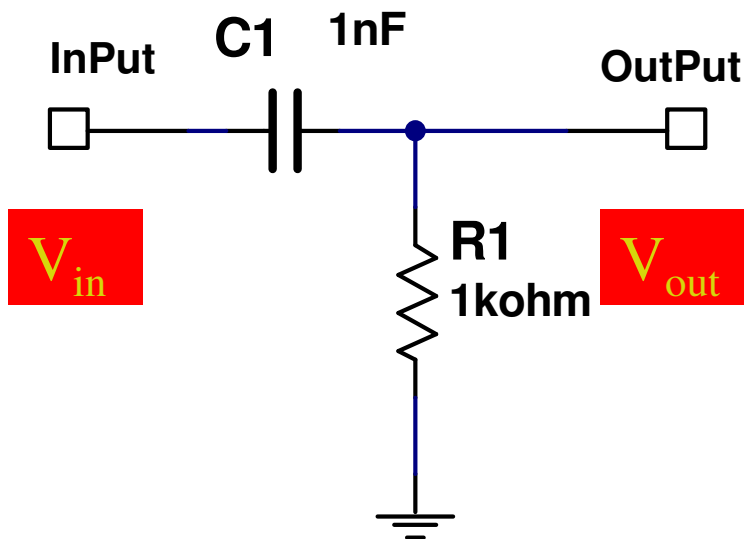

$$I = V_{in} / Z \quad Z = R - i/(\omega C)$$

$$I = V_{in} / (R - i/(\omega C)) \Rightarrow$$

$$V_{out} = V_{in} R / (R - i/(\omega C)) \Rightarrow$$

$$A = V_{out} / V_{in} = R / (R - i/(\omega C)) \Rightarrow$$


$$A = 1 / (1 - i/(2\pi fRC)) \Rightarrow$$

$$A = 1 / (1 - if_0/f)$$

$$A = |A| e^{i\phi} \text{ and}$$




$$|A| = 1 / \sqrt{1 + (f_0/f)^2}$$

$$\tan\phi = f_0/f$$

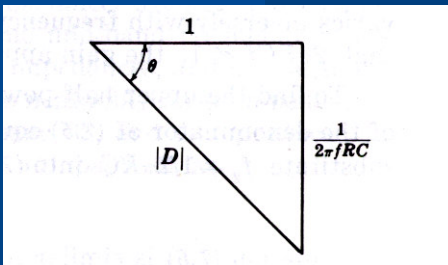



High Pass Filter II

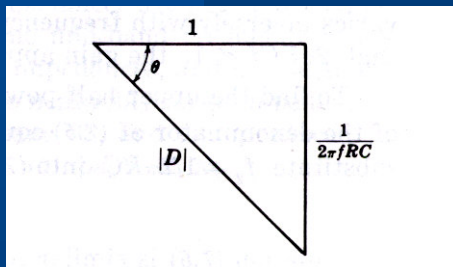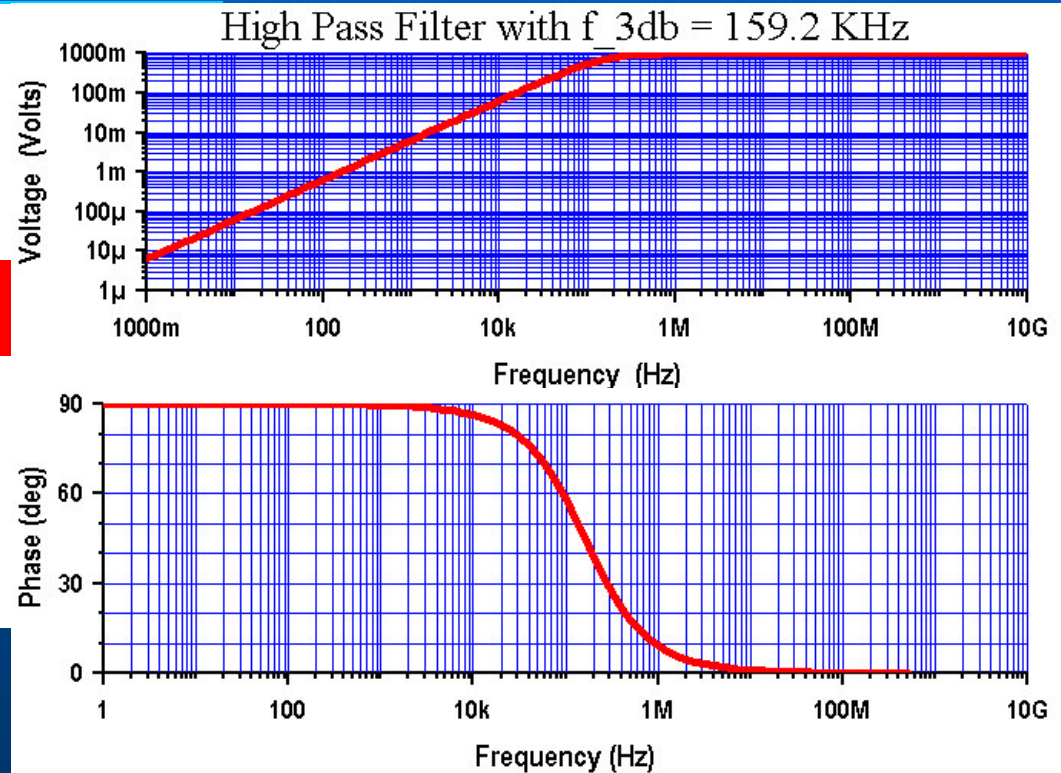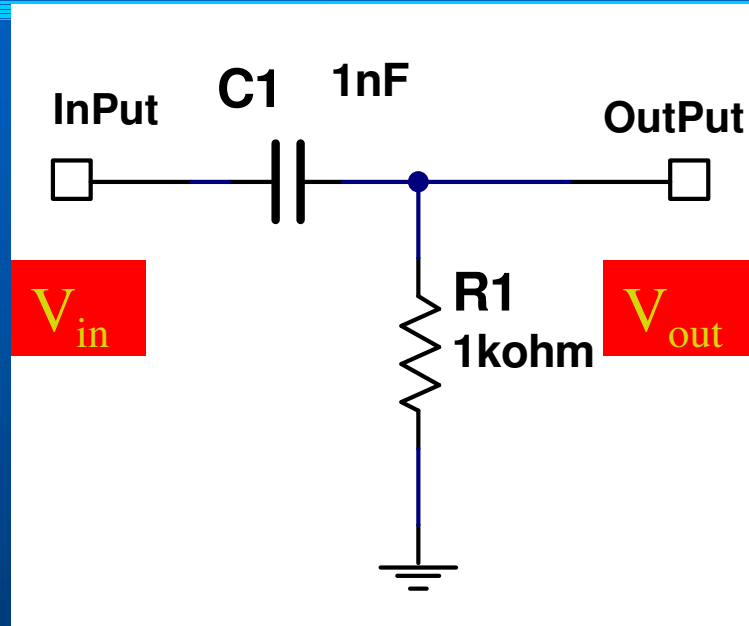

2/19/2004

Costas Foudas, Imperial College,
Rm: 508, x47590


$$\mathbf{A} = |\mathbf{A}| e^{i\varphi} \text{ and}$$

$$|\mathbf{A}| = 1/\sqrt{1 + (f_0/f)^2}$$

$$\tan\varphi = f_0/f$$




High Pass Filter Response III

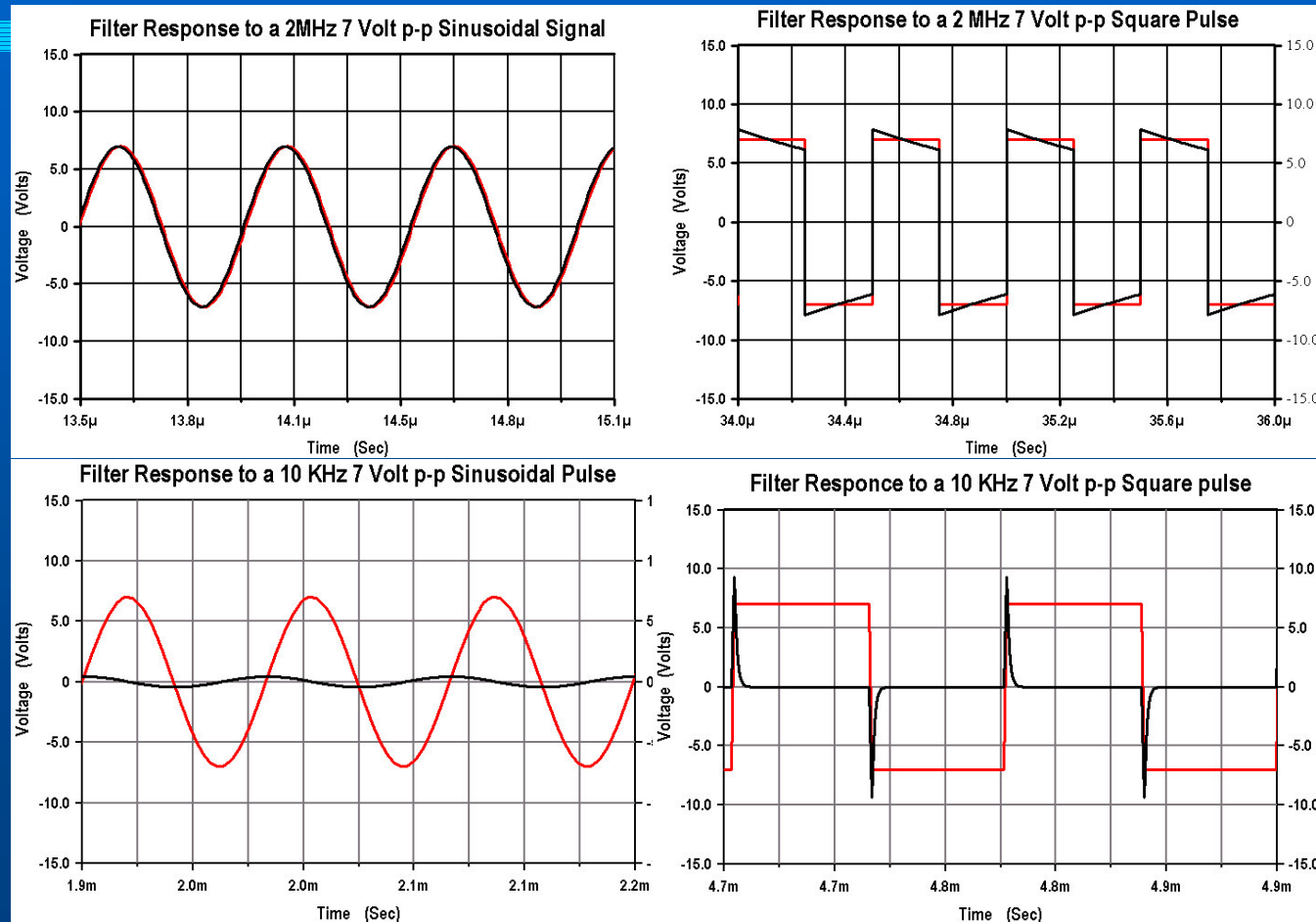



Low Pass Filter I

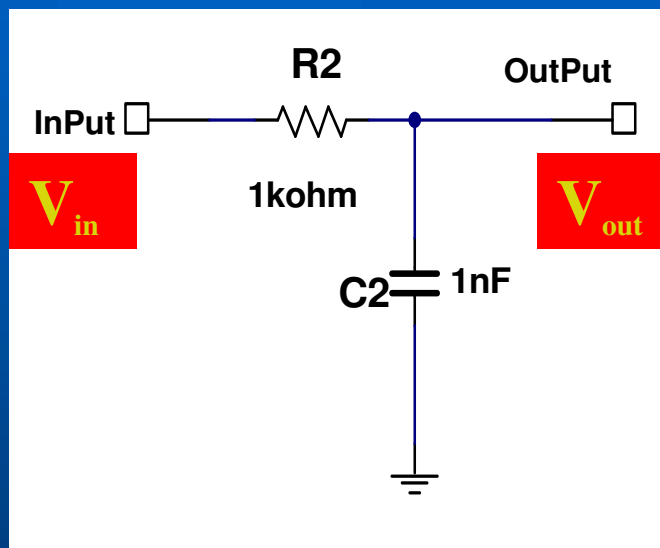

$$I = V_{in} / Z \quad Z = R - i/(\omega C)$$

$$I = V_{in} / (R - i/(\omega C)) \Rightarrow$$

$$V_{out} = V_{in} (-i/(\omega C)) / (R - i/(\omega C)) \Rightarrow$$

$$A = V_{out} / V_{in} =$$

$$- i/(\omega C) / (R - i/(\omega C)) \Rightarrow$$

$$A = 1 / (1 + 2i\pi fRC) \Rightarrow$$

$$A = 1 / (1 + if/f_0)$$


$$A = |A| e^{i\phi} \text{ and}$$

$$|A| = 1 / \sqrt{1 + (f/f_0)^2}$$


$$\tan\phi = -f/f_0$$



Low Pass Filter II


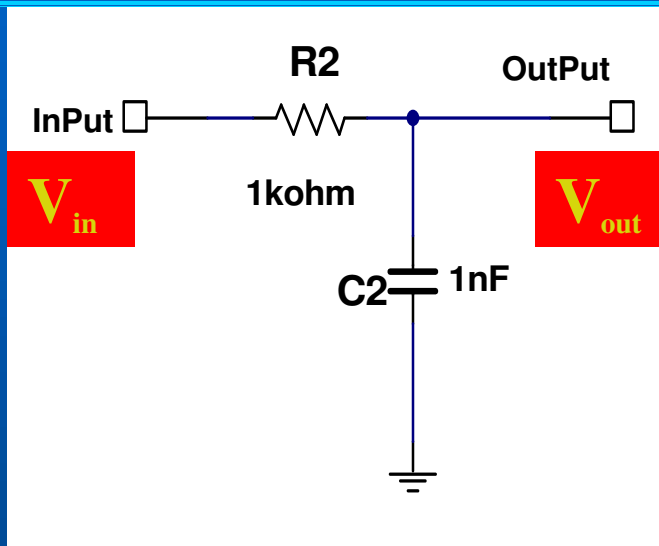


$$\mathbf{A} = |\mathbf{A}| e^{i\varphi} \text{ and}$$
$$|\mathbf{A}| = 1/\sqrt{(1 + (f/f_0)^2)}$$
$$\tan\varphi = -f/f_0$$

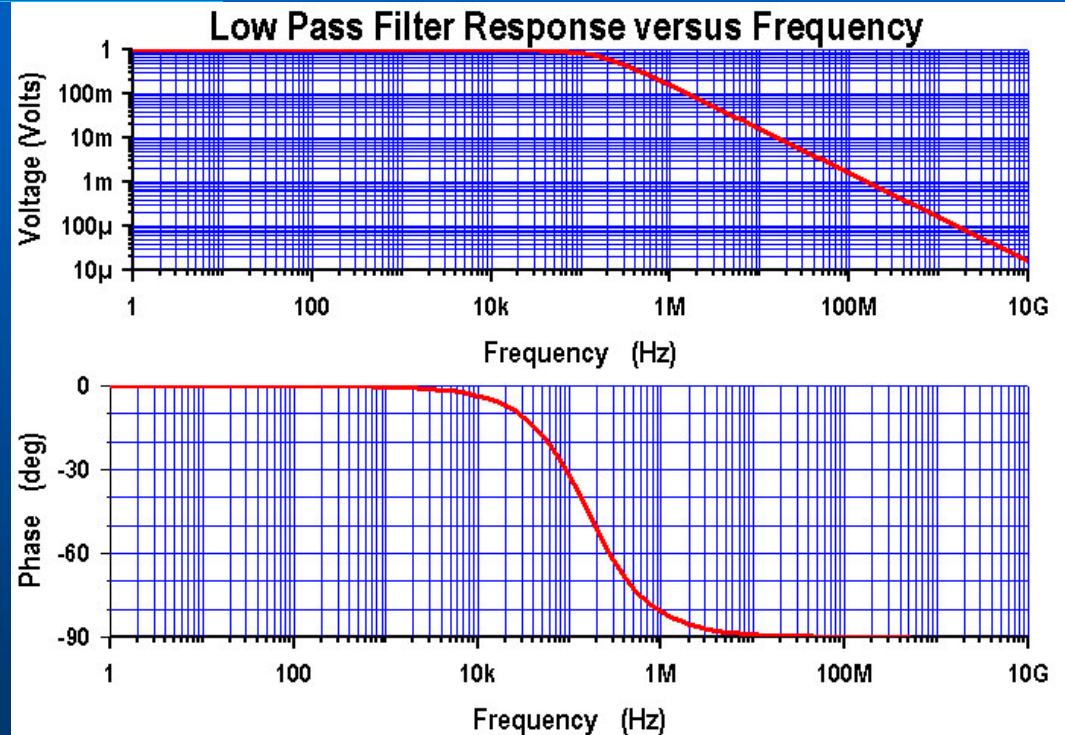




Low Pass Filter Response III

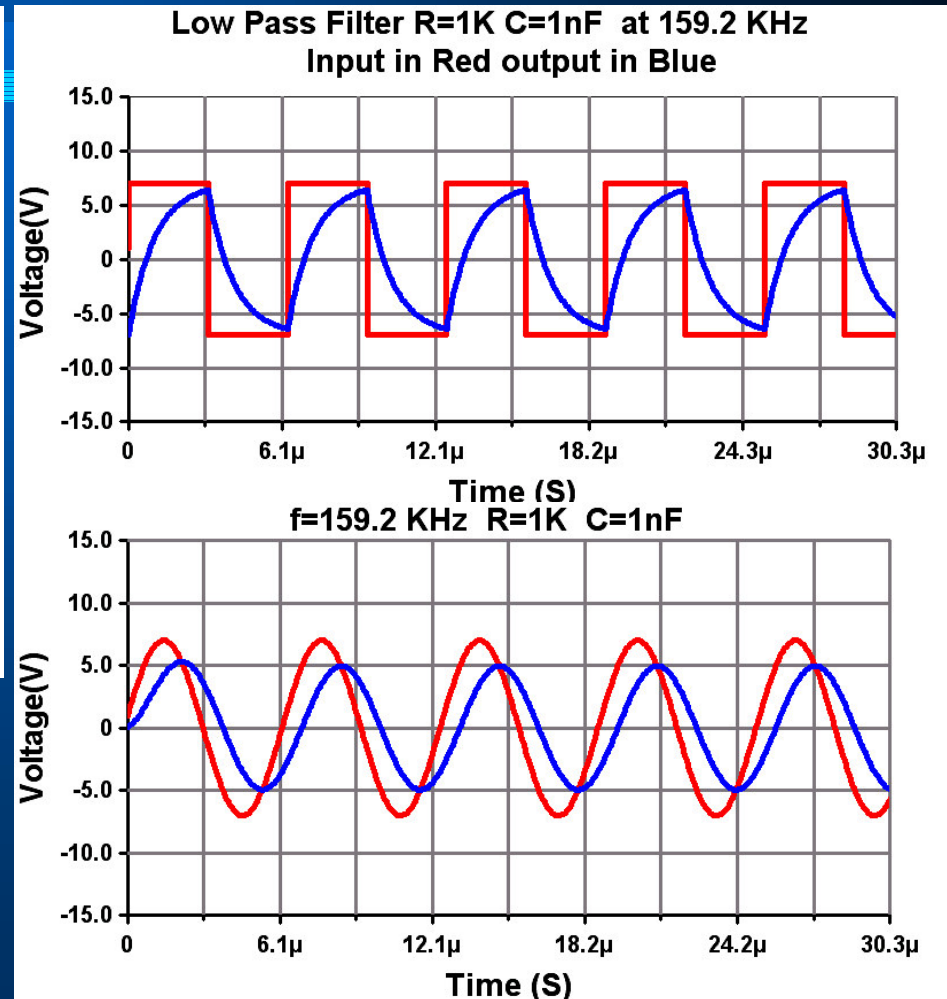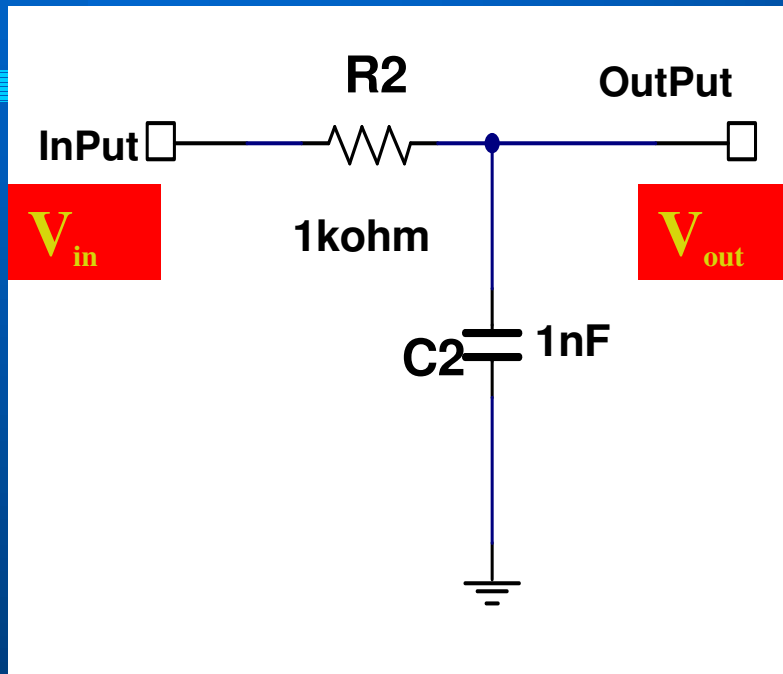




$f_{3\text{dB}}$ of a Filter

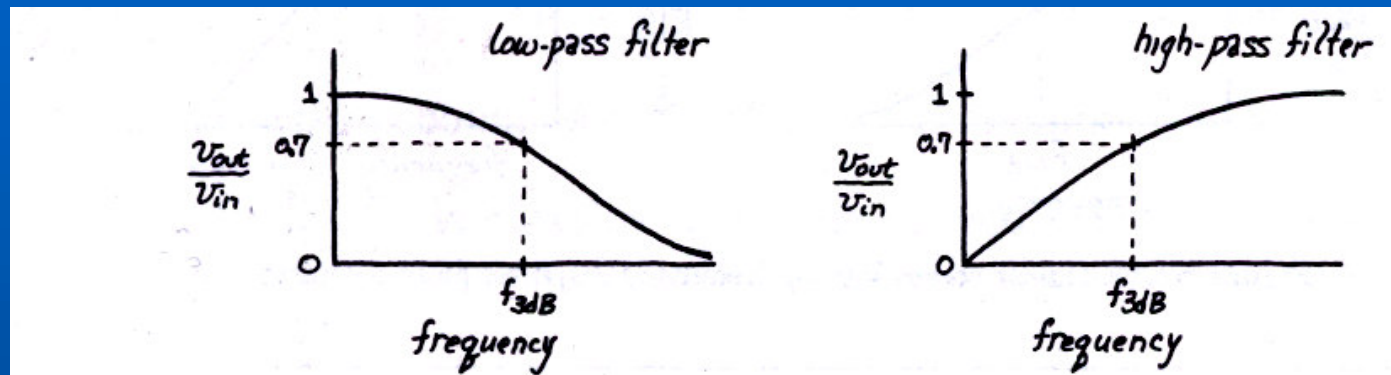

$$f_{3\text{dB}} = 1/(2\pi RC)$$

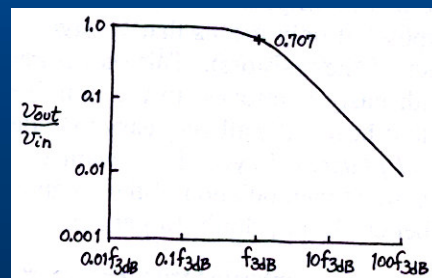


$$\mathbf{A = |A| e^{i\varphi} \text{ and}$$
$$\mathbf{|A| = 1/\sqrt{(1 + (f_0/f)^2)}}$$
$$\mathbf{\tan\varphi = f_0/f}$$

$$\mathbf{\text{If } f_0=f \text{ then } |A|=1/\sqrt{2} = 0.707}$$



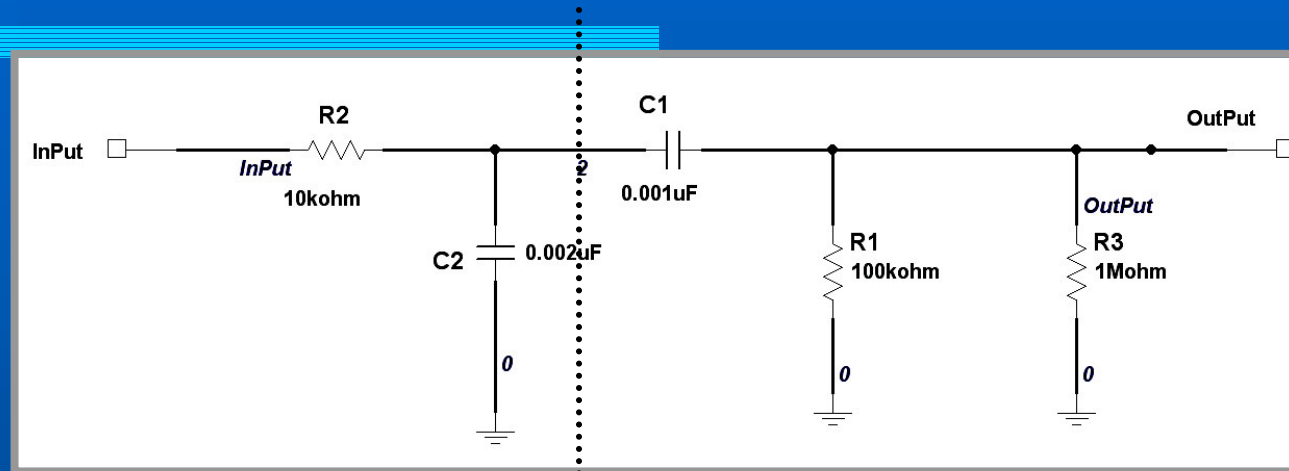Design a Band-Pass Filter for 1.6-8 KHz ; 1M Ω



Low Pass

High Pass

Pick $R_1 = (1/10) 1 \text{ M } \Omega = 100 \text{ K } \Omega$
and $R_2 = (1/10) R_1 = 10 \text{ K } \Omega$

$$f_{3\text{dB}} = 1/(2\pi RC) \Rightarrow$$

$$C2 = 0.002 \mu \text{ F}$$
$$C1 = 0.001 \mu \text{ F}$$



Band Pass Filter Response

- It cuts both high and low frequencies whilst it keep a predetermined range of frequencies:

