

# Transistors


2/19/2004

Costas Foudas, Imperial College,  
Rm: 508, x47590

1



# Review : What is a Transistor ?

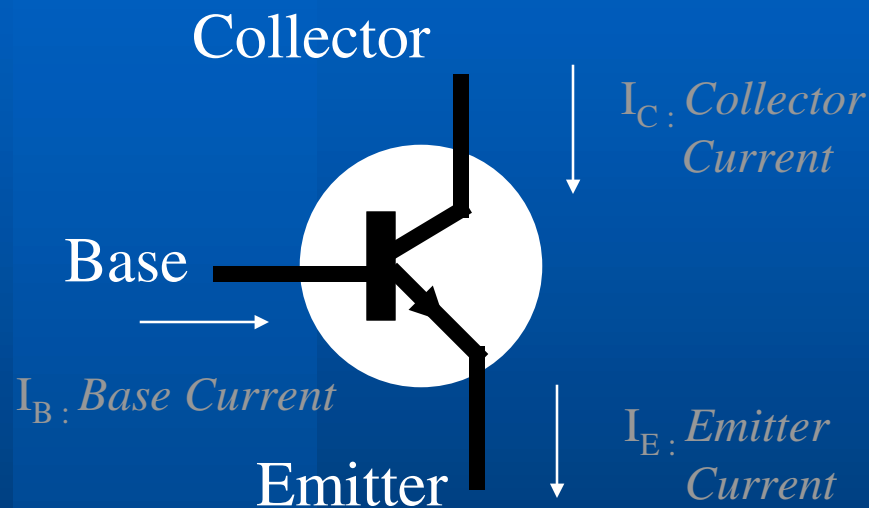

## NPN Transistor Rules:

$$V_C > V_E$$

$$V_B = V_E + 0.6 \text{ Volts}$$

$$I_C = I_B * \beta$$

$$I_E = I_C + I_B \Rightarrow$$

$$I_E = (1 + \beta) I_B$$

FOR MORE INFO...

Relevant Books: Art of Electronics + Lab: *Harowitz and Hill*


Electronic Circuits: *E.C. Lowenberg, SCHAUM SERIES*

Electric Circuits: *J.A. EDMINISTER SCHAUM SERIES*




# Some Transistor Applications I

- Follower:

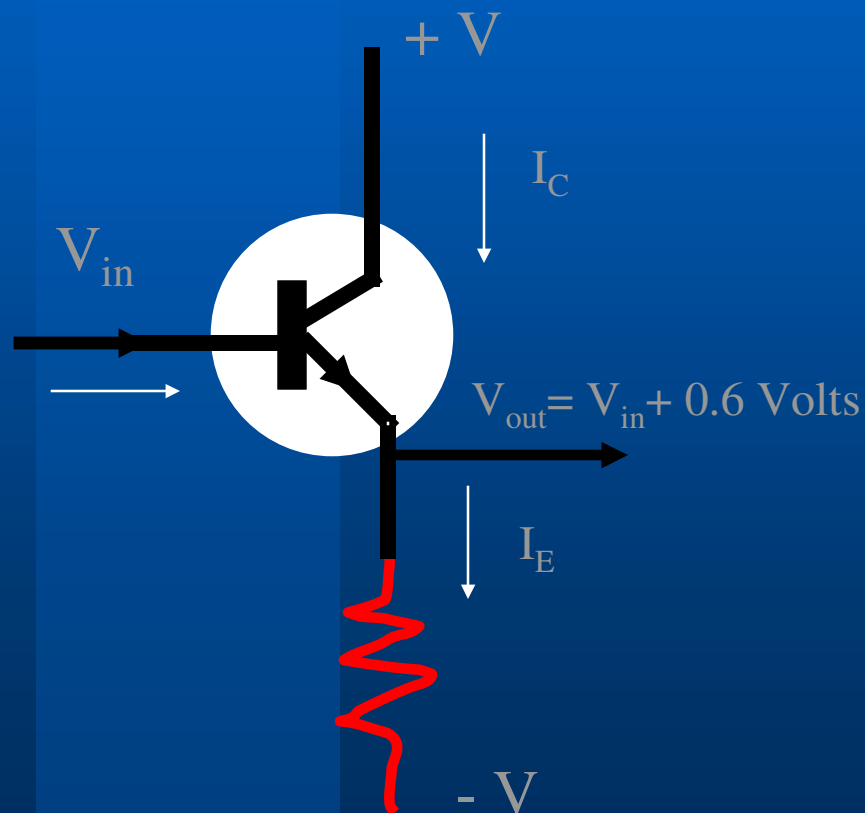


- Current Source

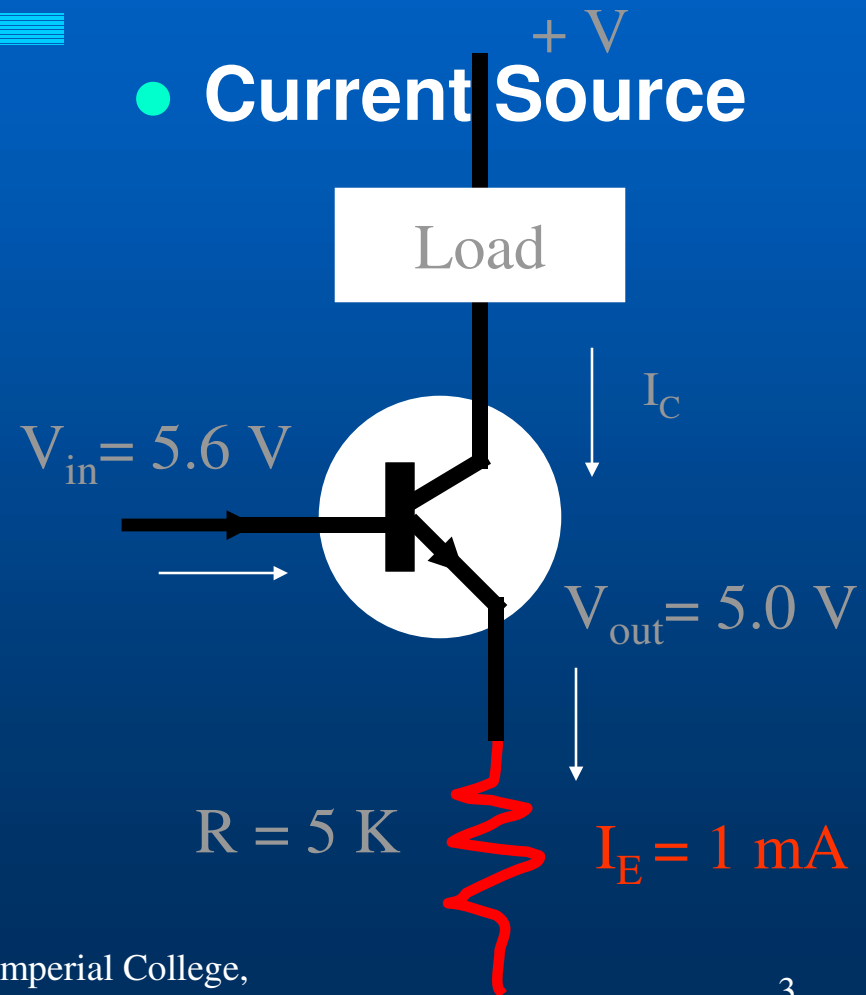




# Some Transistor Applications II

- Common Emitter Amplifier :

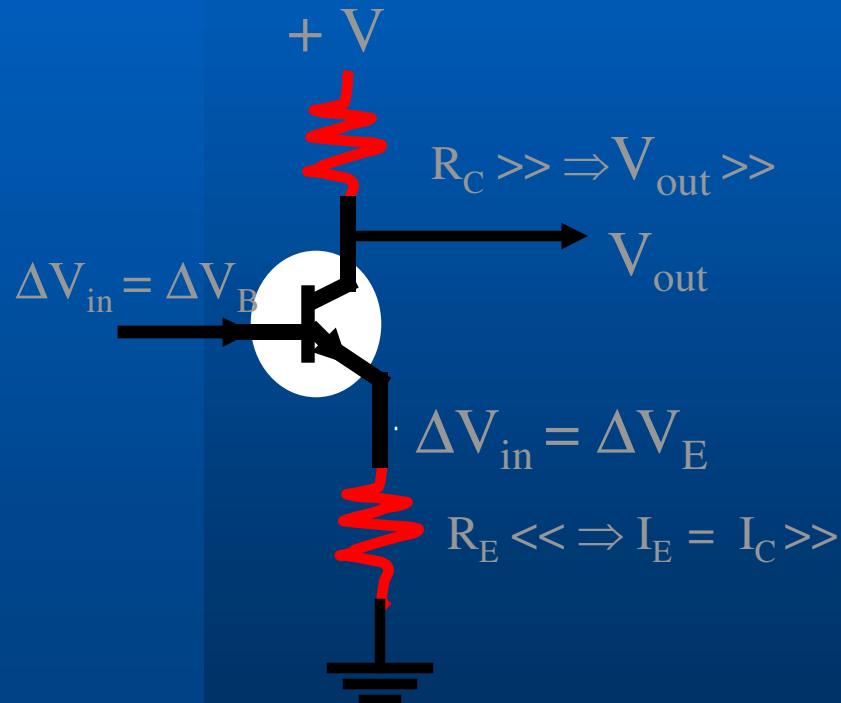

- Push-Pull :

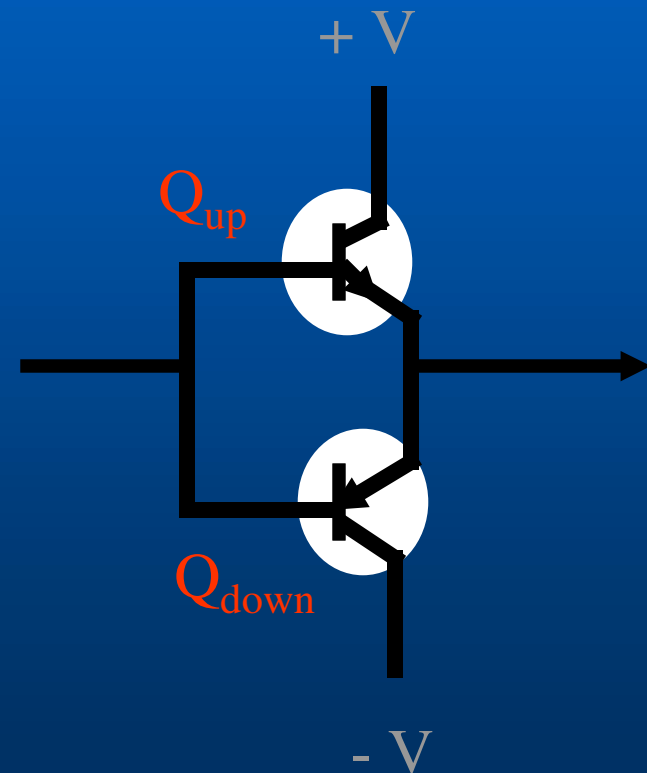



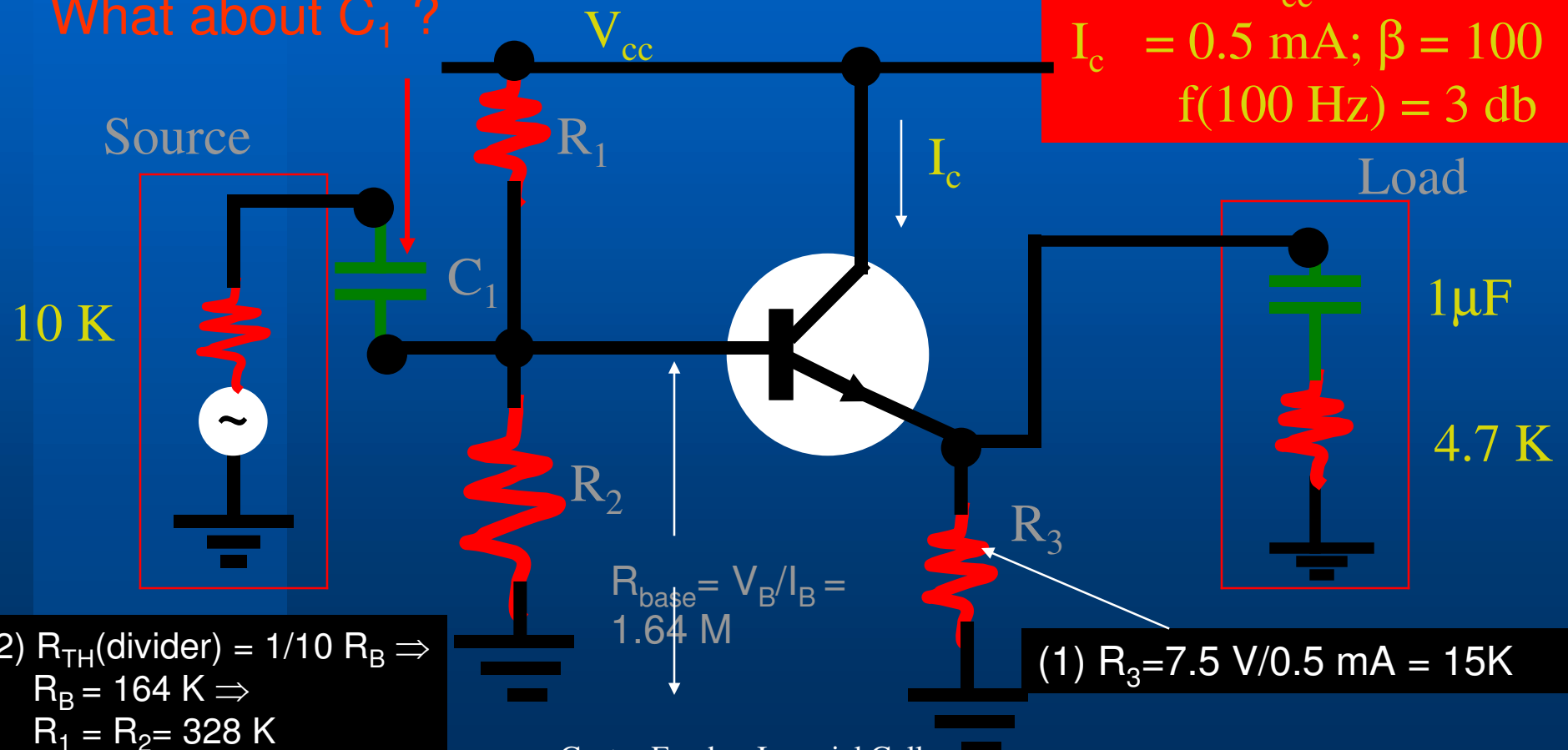
# The Emitter Follower I

What about  $C_1$  ?

Given :  $V_{cc} = 15$  Volts  
 $I_c = 0.5$  mA;  $\beta = 100$   
 $f(100 \text{ Hz}) = 3 \text{ db}$




2/19/2004

Costas Foudas, Imperial College,  
Rm: 508, x47590




# The Emitter Follower II

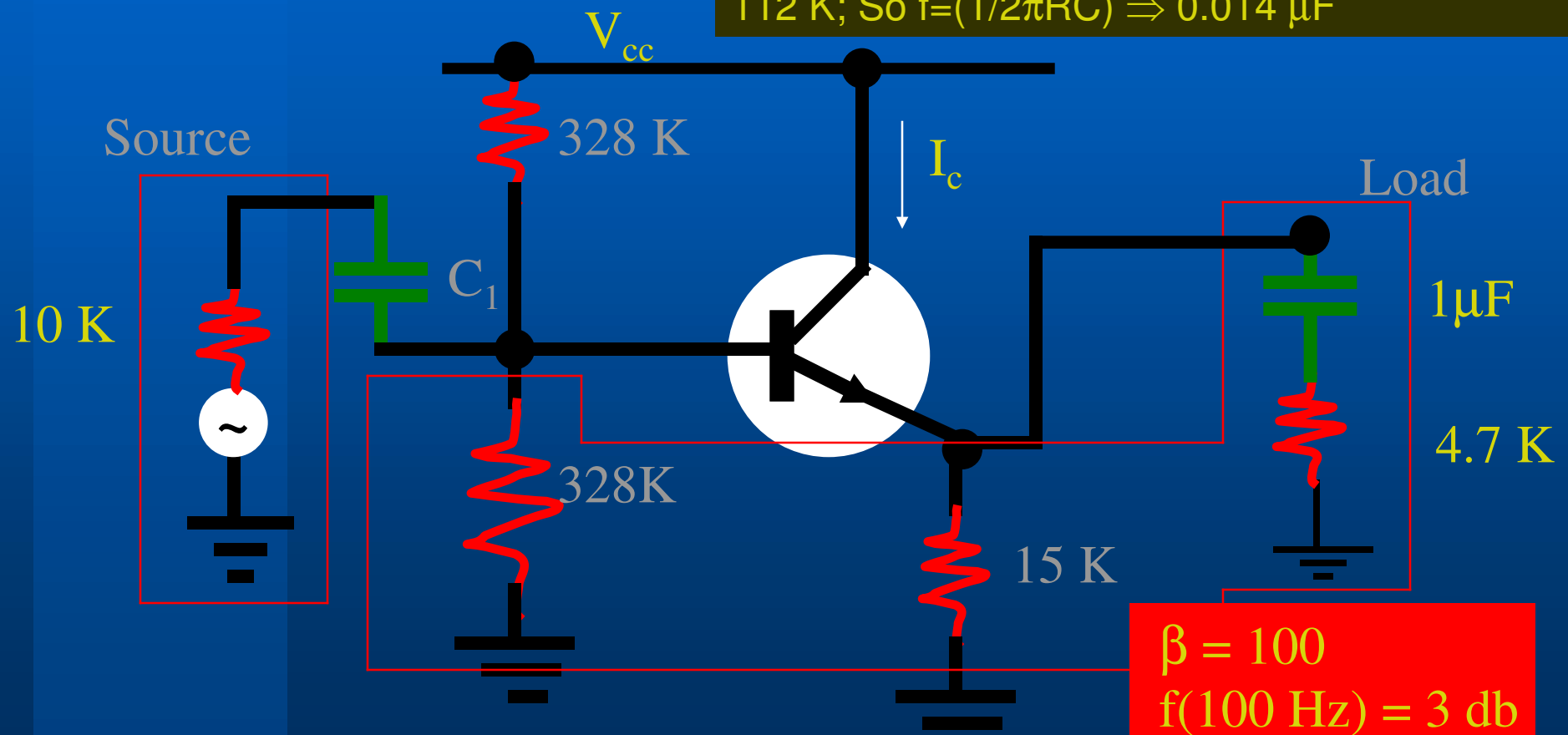(3) Think of an RC filter (high-pass) .  
15K is parallel to 4.7 K and the whole think times  $\beta$   
 $\Rightarrow 358 \text{ K}$  ; parallel with 328 K  $\Rightarrow$   
112 K; So  $f=(1/2\pi RC) \Rightarrow 0.014 \mu\text{F}$





# Emitter Follower (a bit diff.)

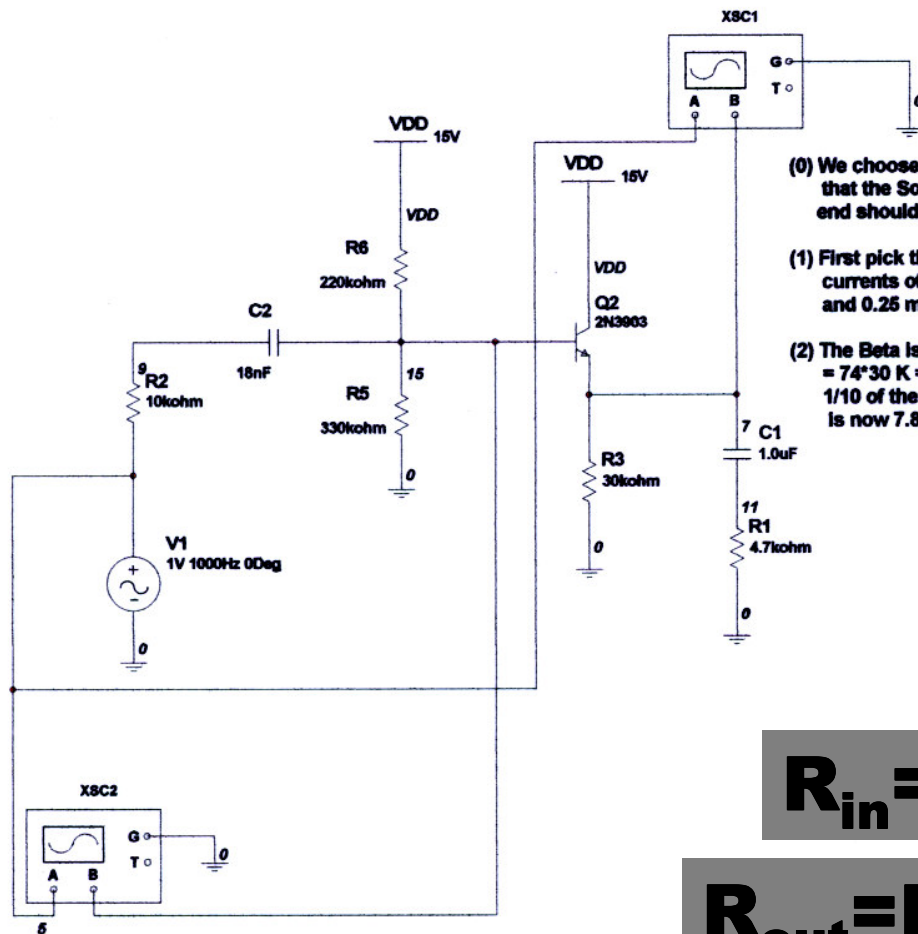


- (0) We choose to operate the output at about 7.5 Volts. Note also that the Source has an impedance of 10 K so the receiving end should have at least a factor of 10 larger impedance.
- (1) First pick the Collector Current: 2N3903 can operate up to currents of 200 mA. We choose ~0.250 mA as opeartion point and 0.25 mA x 30 K is 7.5 Volts..If not we can correct it later.
- (2) The Beta is measured to be 74...base input resistance =  $74 \times 30 \text{ K} = 2.22 \text{ MOhm}$ ; Thevenin divider = 132 K less than 1/10 of the Base Emitter input resistance; the output voltage is now 7.847 Volts and  $V_{be} = 8.475 \text{ Volts}$

$$R_{in} = R_{load}(1 + \beta)$$

$$R_{out} = R_{source} / (1 + \beta)$$



# Common Emitter Amplifier

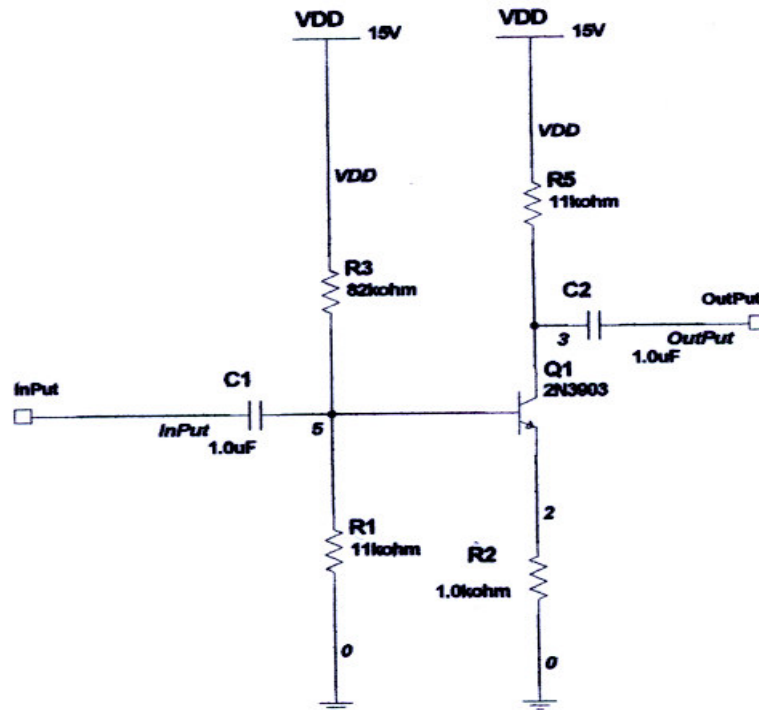

$$\text{Gain} = R_5/R_2$$

$$R_{\text{out}} = R_5$$





# Common Emitter Amplifier II


## Problem: common emitter amp

Design a common-emitter amp to the following specs:

- $V_+ = 20V$
- $f_{3dB} = 100 \text{ Hz}$  (approx.)
- gain = -100 at quiescent point.
- $I_C$  quiescent = 0.5 mA
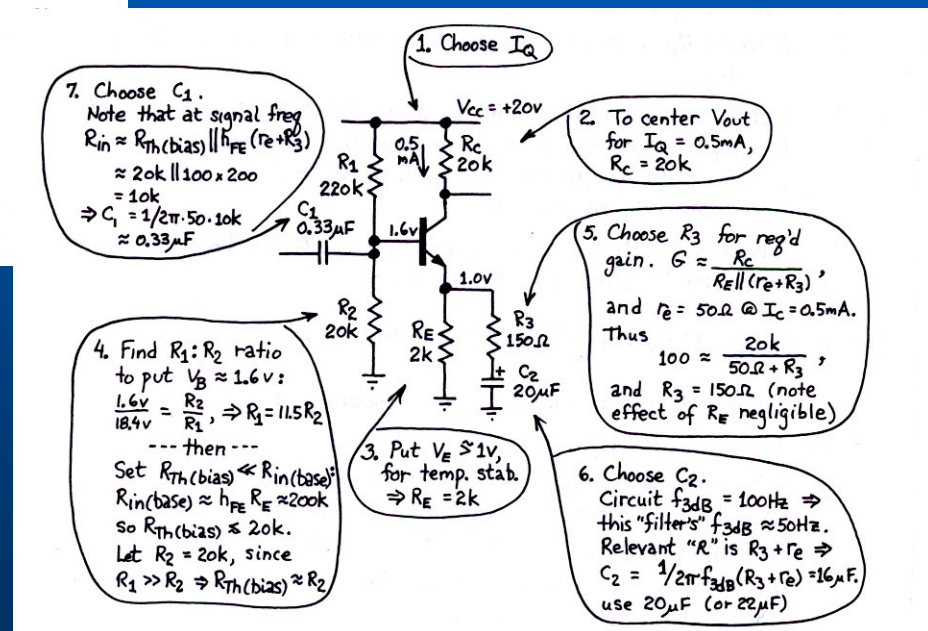
## Questions:




- What is the amp's gain—
  - when the output swings to about +15V?
  - when the output swings to about +5V?
- What is the amp's  $Z_{out}$ ?




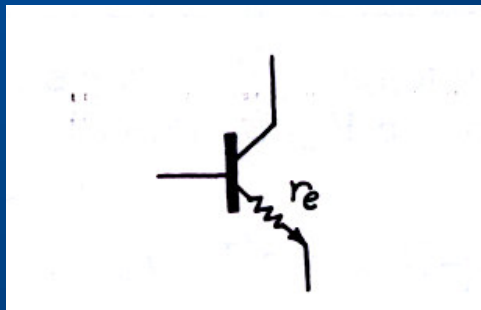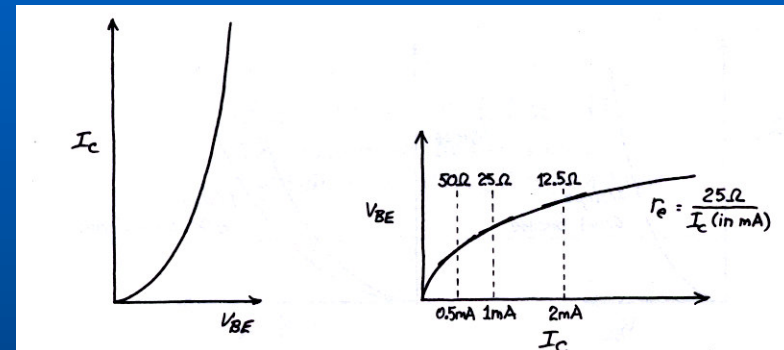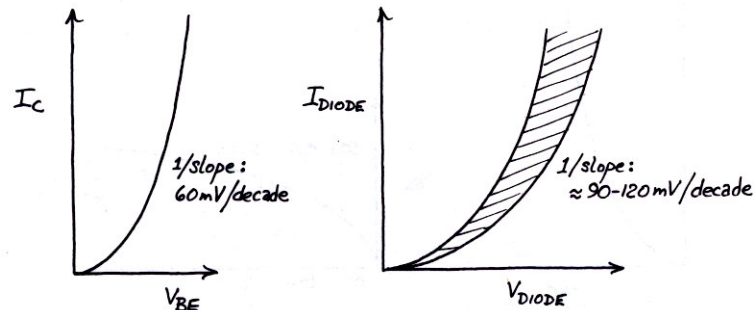
# The Ebers-Moll Model for BJT

Class 5: Tr II: Corrections to the first model: Ebers-Moll



Ebers-Moll

$$I_C = I_S (e^{V_{BE}/(kT/q)} - 1)$$

(grows fast with temperature; more on this later)

(negligible)

Ignoring the “-1” term, we can say simply that  $I_C$  grows exponentially with  $V_{BE}$ .


In addition, we might as well plug in the room-temperature value for that complicated expression “ $kT/q$ ,” 25 mV. Then Ebers-Moll doesn’t look so bad:

Ebers-Moll: (slightly simplified)

$$I_C \approx I_S e^{V_{BE}/25\text{mV}}$$



# Temperature Effects

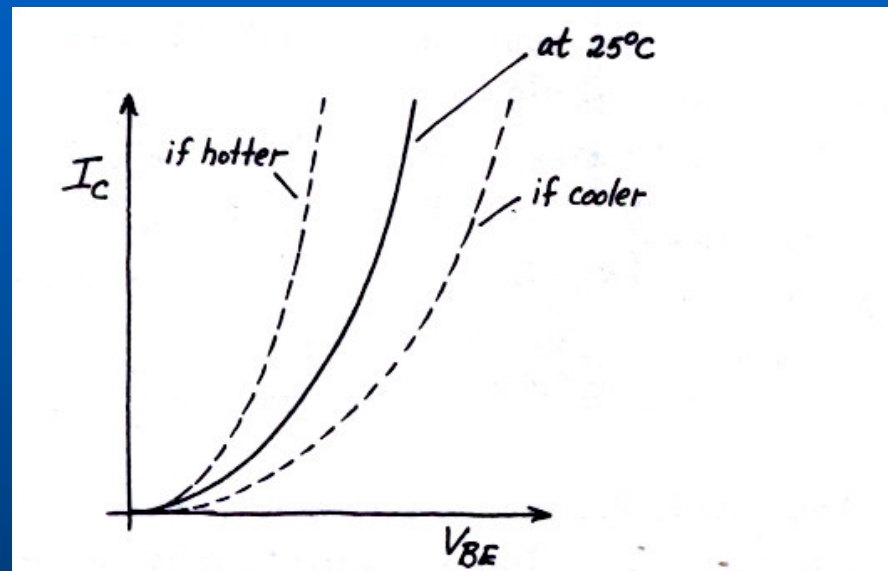


## Temperature Effects: *two equivalent formulations*

- $I_C$  grows at about 9%/°C, if you hold  $V_{BE}$  *constant*.
- $V_{BE}$  falls at 2mV/°C, if you hold  $I_C$  *constant* (This is the text's formulation.)


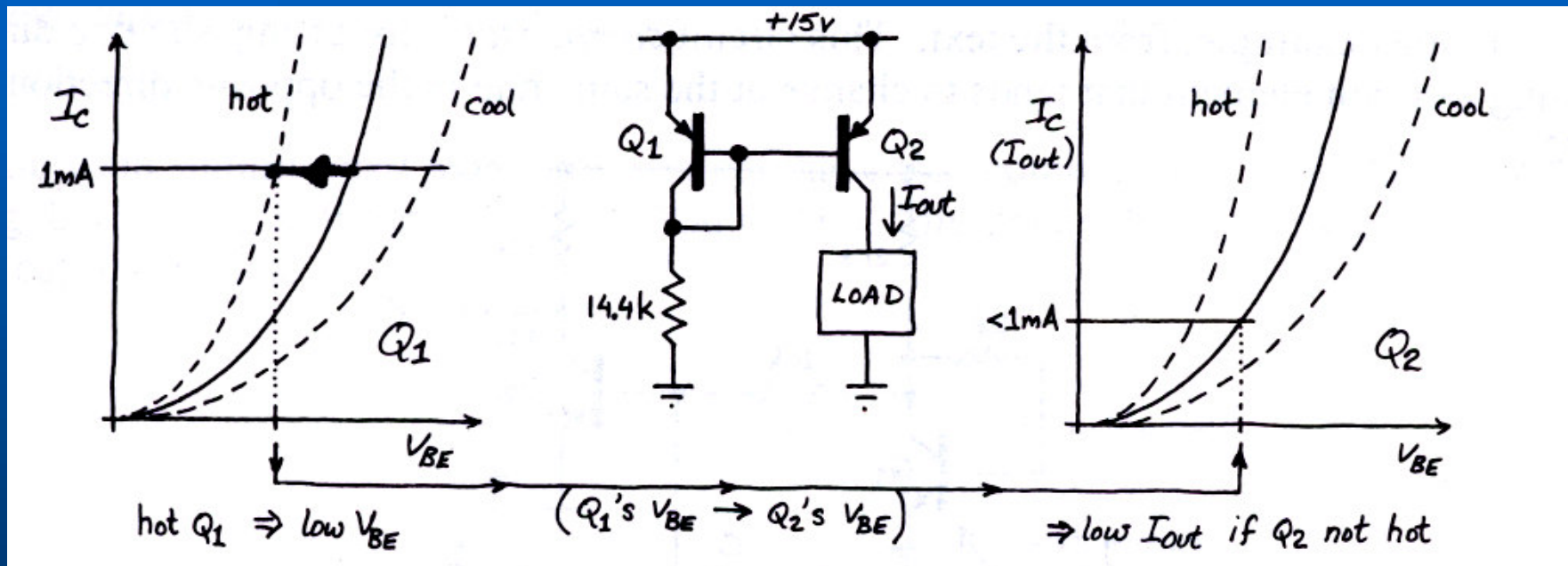
# Temperature Effects and Current Mirrors






# Exercises

- **Make a Current Source using a transistor**
- **Make common emitter follower**
- **Make a Common Emitter Amplifier**




# Making Gates using Transistors I

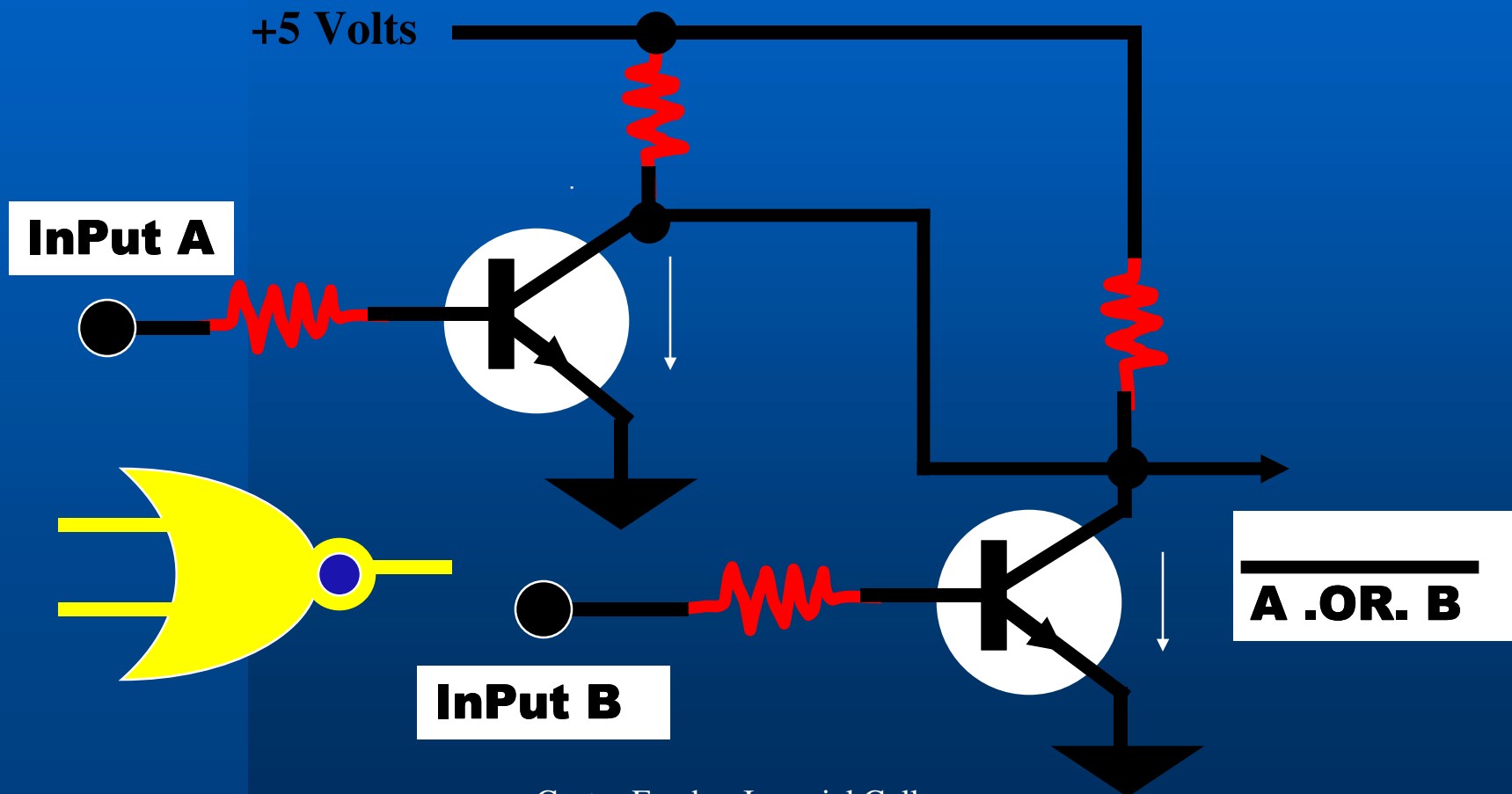



# Making Gates using Transistors II

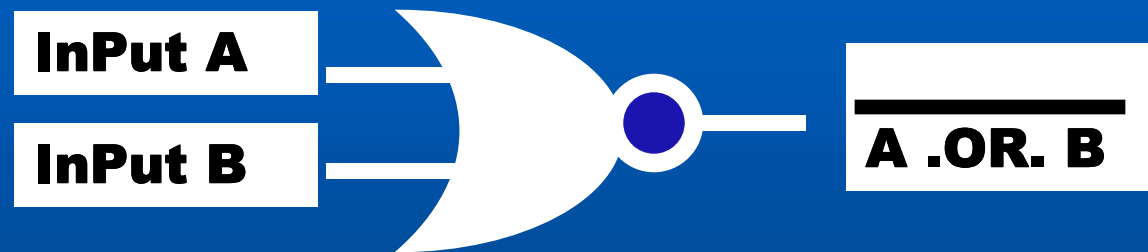


**Here is  
what we  
have made**

A	A	OUT
1	0	0
1	1	0
0	1	0
0	0	1



# Exercise I

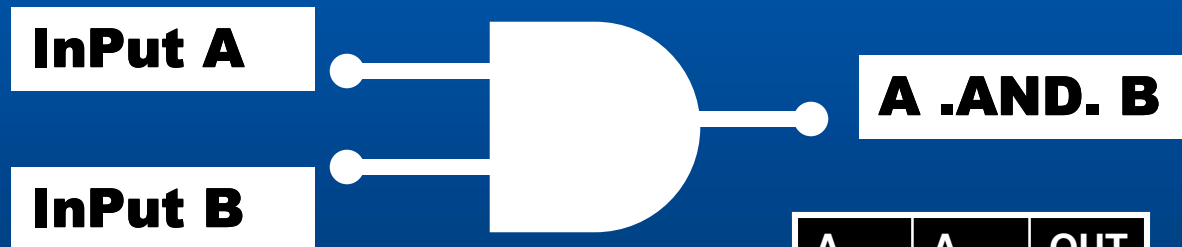**Design and construct an AND gate using transistors and resistors :**



**The AND gate  
TRUTH table**


A	A	OUT
1	0	0
1	1	1
0	1	0
0	0	0





# Exercise I continued

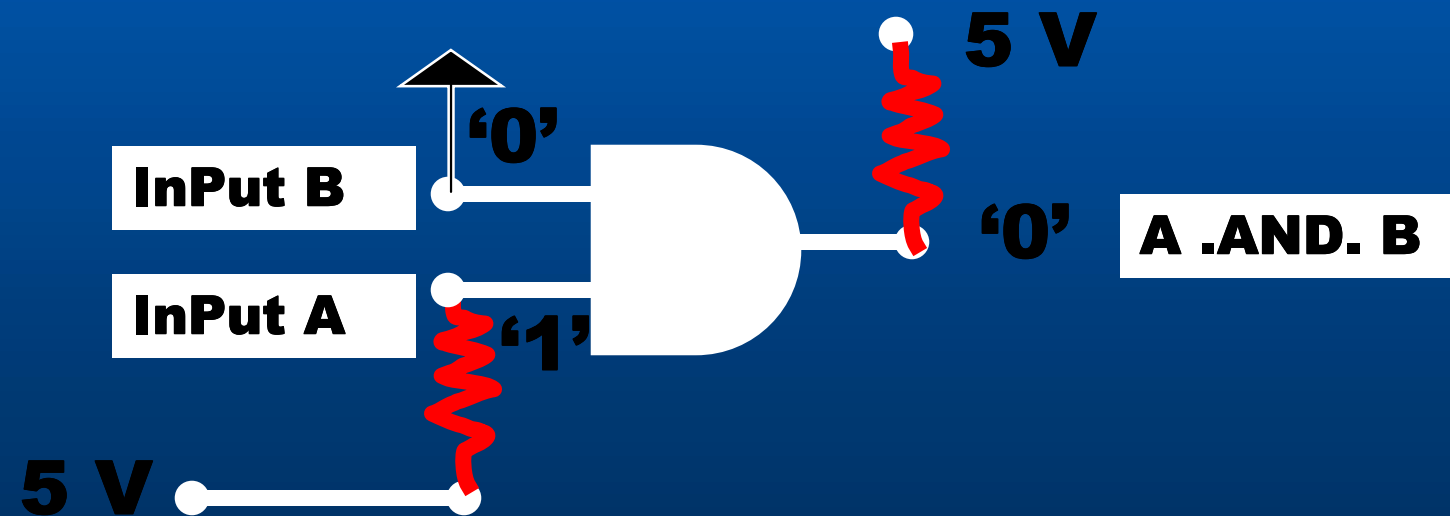
**Verify the truth table ! You can set an input to '1' by connecting it to +5 V by a resistor of 1K and you set it to '0' by grounding it.**






# Answer (almost):

## TTL

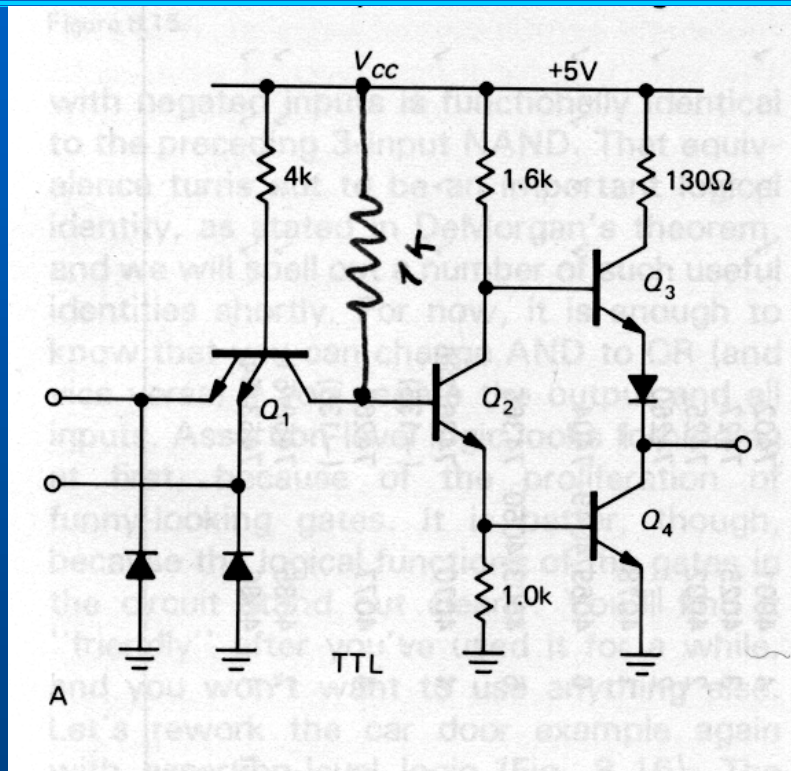

## CMOS

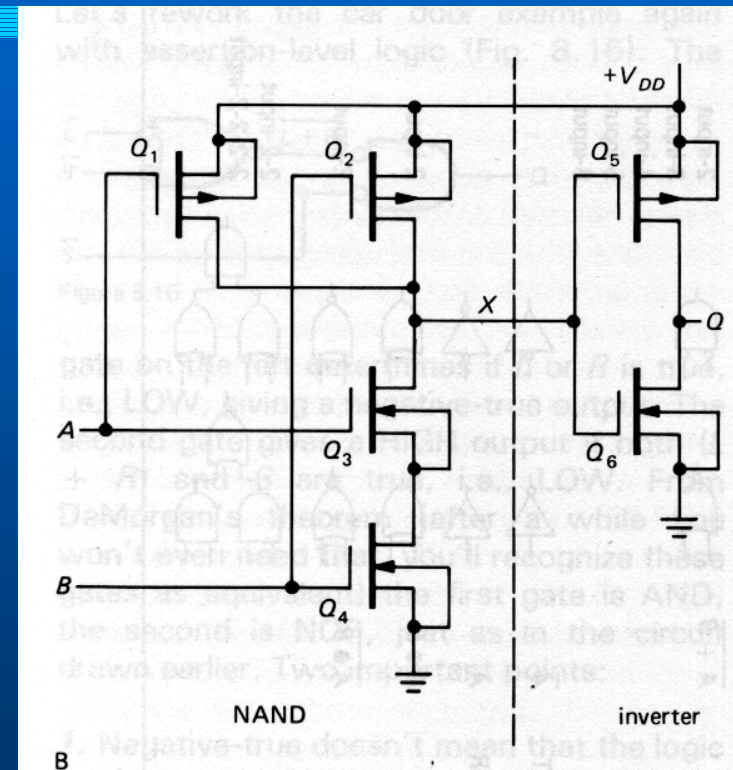

**Not quite because this is a NAND gate but we do know  
by now how to invert using a transistor**



# Important conclusion

**You may understand by now  
that the inputs have no  
ability to set signals high or  
low. In contrast to this the  
outputs can drive signals to  
High or Low**



# Remember:

**Inputs draw no current.  $1\text{K}\Omega$  resistors to +5 V can set inputs to high or they can be set low by connecting to ground.**

**Outputs can draw current and can force lines to low or high.**