

### **Junction** Diodes

- Most elementary solid state junction electronic devices.
- They conduct in one direction (almost correct).
- Useful when one converts from AC to DC (rectifier).
- But today diodes have a wide range of applications from LEDs, photodiodes, a variety of sensors and in optical communication







### The Diode Symbol

- The Diode Symbol:
- Current flows from Anode to Cathode





- This is how they look :
- Anode (Higher V)
- Cathode (Lower V)

2/18/2004





2/18/2004

Costas Foudas, Imperial College, Rm: 508, x47590

3



#### **Forward Bias Characteristics**



In 'forward bias' the diode draws current according to: Is called <u>Saturation Current</u> V is the Diode Voltage  $V_{T} = KT/q = 25.2 \text{ mV}$  at T=20 C<sup>0</sup> K = 1.38 10<sup>-23</sup> Jules/Kelvin (Boltzmann's constant)  $q = 1.6 \ 10^{-19} \ Cb$ n = 2 for discrete components n = 1 for diodes within ICs

Costas Foudas, Imperial College, Rm: 508, x47590

2/18/2004



#### Voltage Drop vs Current

• One can solve for V(I):

- $I(V) = I_{S} \{ e^{(V/nV_{T})} 1 \}$
- to get  $V_2 V_1 = nV_T ln(l_2/l_1)$
- or  $V_2 V_1 = 2.3 \text{ nV}_T \log(I_2/I_1)$

 <u>Conclusion</u>: A factor of 10 in current results to 60 mV in voltage drop (n=1) or 120 mV n=2



# Temperature Dependence (1N4001 in forward bias)

- Both I<sub>S</sub> and the exponent are temperature dependent in
  - $I(V) = I_{S} \{ e^{(V/nV_{T})} 1 \}$
- In fact most of the temperature dependence comes from I<sub>s</sub>
- Rule : -2 mV per <sup>0</sup>C



2/18/2004





### Diodes in reverse bias

 In reverse bias the V<0 and as it becomes more negative the exponential term vanishes

 $I(V) = I_{S} \{ e^{(V/nV_{T})} - 1 \} \Rightarrow I_{R} = I_{S}$ hence the name 'saturation'.  $I_{S} = 10^{-14} - 10^{-15} \text{ A}$ 

 In practice the reverse current is much larger, of the order of nA, because of leakage effects which dominate and have different temperature dependence.

 Rule of thumb: <u>I<sub>s</sub> doubles every 5 <sup>o</sup>C</u> <u>In reality</u> <u>I<sub>R</sub> doubles every 10 <sup>o</sup>C (leakage</u>)





#### **Exercise 1-I: Simple Rectifier**



Only the positive part of the signal (shown in red) goes through
But the output is hardly DC....

> Costas Foudas, Imperial College, Rm: 508, x47590

2/18/2004



#### **Exercise 1-II:** Add 5µF Capacitor



- Assume a output current of I<sub>out</sub> = 1 mA
- When the supply voltage is below ~ V<sub>out</sub> 0.7 the diode stops conducting and the capacitor discharges through the load resistor
- What capacitor do I need for 1% ripple noise ( = 55 mV)?



### Exercise 1-III: Calculating C



$$Q = CV \implies \frac{dQ}{dt} = C \frac{dV}{dt} \implies T_c = C \frac{dV}{dt}$$
Dulking the discharge phase  $T_c = T_p$   $(T_p = S)$ 

$$\therefore \quad \frac{V}{R} = C \frac{dV}{dt} \implies \frac{dV}{dt} = \frac{V}{RC} \implies Assume that RC >> T \implies V = V_0$$
(ideal diode)

$$\frac{\partial V}{\partial t} = \frac{V_0}{RC} \Rightarrow \Delta V = V_{ripple} = \frac{V_0}{RC} \Delta t \stackrel{\Delta t \approx T}{\Rightarrow}$$

$$V_{ripple} = \frac{V_0 T}{RC} = \frac{V_0}{fRC}$$

$$C = \frac{V_0}{fRV_{ripple}} = \frac{100}{50 \times 5.510^3} F = 363.6 \mu F$$
This calculation is

This calculation is only valid when RC>>T
Notice that when C = 5µF this approx. is not valid.

Costas Foudas, Imperial College, Rm: 508, x47590

2/18/2004

10



### Exercise 1- IV: $C = 363.6 \mu F$



#### **Exercise 1-VI:** Average Diode Current



2 Example: SOMA N 50H2  $V_{t} = \frac{V_{p}}{\int RC} = \frac{260 V}{50 \text{ sec}^{2} \text{ Alo}^{2} \text{ so } 10^{6} \text{ F}} = \frac{1}{50} 10^{3} \text{ Volts}$ Ve= 20 Volts  $I_{D}^{AVERAGE} = \frac{200V}{4K^{2}} \left[ 1 + 3.14 \right] \frac{2200}{20} \right]$ I AVERAGE = 752 mA : Although we only drow SOMA one diode Meeds to be able to survive ISIMA average currents!! Average Current 752 mA

Costas Foudas, Imperial College, Rm: 508, x47590

2/18/2004



#### **Exercise 1-VII: Maximum Diode Current**





#### Maximum Current 1.5 A

Costas Foudas, Imperial College, Rm: 508, x47590



# Exercise 1- V: Bridge Supply



- The Diode Bridge utilises both the positive and the negative part of the AC pulse.
- Hence, rectifying such a signal is easier and a smaller capacitor (half as big) does the same job.

2/18/2004





- Since the output of the bridge rectifier has a period which is half the period of the one diode rectifier we need a filter capacitor which is half as large.
- The ripple voltage is shown to be 37 mV (even better than before).

#### Exercise 2: AND Gate



- Diodes in AND gate configuration.
- One input disconnected (floats)
- The output (red) is 0.7 Volts shifted from the input (blue)



#### **Clipping Circuits** with Diodes



 Often one needs to limit the range of some input analogue pulse or even to clip spikes on a digital signal.
 This can easily be done with a diode and a voltage source



#### Voltage Doubling Circuits



- C1 Charges during the first half of the reverse phase.
- C1 is in series with the source during the forward phase. Hence it doubles the output voltage.
- The output voltage will approach to 2\*V1-2\*V<sub>D</sub>



#### Costas Foudas, Imperial College, Rm: 508, x47590

2/18/2004



#### Voltage Doubling Circuits



Hence, the time it takes to stabilize can also be calculated

2/18/2004



- Here is the proof that the first step is V/2
- The next step can be calculated: V<sub>D</sub> ≈ 0.7 Volts but you need the diode equation in order to calculate the current and then the charge...



### **Appendix I:** Semiconductors

 For those of you who are interested to see how the diodes and in general the semiconductors work.

• For the students who are not taking the Instrumentation course.

2/18/2004



- What us a p-type and what is an n-type semiconductor
- Electrical properties of semiconductors



# Semiconductor Physics II Silicon Lattice

- Silicon atoms are held in place by 4 covalent bonds.
- At sufficiently low Temperature there are no free electrons or holes (carriers)
- At room temperature some bonds brake (thermal excitation) and *n* free electrons and *p* holes are created.
- $n = p = n_i$



Bound electrons

Silicon



### Semiconductor Physics III

- The number of carriers n<sub>i</sub> is obviously temperature dependent:
- $n_i^2 = BT^3 e^{(-E_G/KT)}$  (proof in App. II)
- B= 5.4 10<sup>31</sup> K<sup>-3</sup> cm<sup>-6</sup>
- E<sub>G</sub> = 1.12 eV (Si)
- K = 8.62 10<sup>-5</sup> eV/K
- At 300 K n<sub>i</sub> = 1.5 10<sup>10</sup> to be compared with 5 10<sup>22</sup> Si-Atoms/cm<sup>3</sup>
- The semiconductor conductivity rises with temperature



# Semiconductor Physics IV Energy Bands

- Metals have no gap between the conduction band and the last bound band.
- Insulators have a large gap
- Semiconductors have a small gap ~ 1eV
- At T>0 thermally excited electrons move to the conduction band leaving holes behind.



2/18/2004



# Semiconductor Physics III Diffusion Current

- The net current created by thermal excitation is of course zero because the motion is random and the silicon carrier density is uniform.
- But suppose that the carrier density is made non-uniform.
- In this case the thermal excitation results to the <u>Diffusion Current</u>: I<sub>D</sub>.





# Semiconductor Physics IV Drift Velocity and Current

- The carriers (electrons/holes can also drift under the influence of an electric field E.
- The Drift velocity is proportional to the Electric field but different for electrons and holes:



# • The constant $\mu_p$ is the mobility for electrons and $\mu_n$ the mobility for holes

2/18/2004



Semiconductor Physics V Drift Current Density

- For Si the electron mobility is 1350 cm<sup>2</sup>/Vs and the hole mobility is 480 cm<sup>2</sup>/Vs.
- From first year physics one can calculate that the <u>current density</u> due to the drift velocity is:



# **Doped Semiconductors (VI)**

- Doped semiconductors come either as n- or p-type (electrons or holes are predominately the carriers)
- Introducing small Phosphorus (which has 5 valence electrons) impurities generates an n-semiconductor since one electron remains free. Hence Phosphorus is a <u>Donor.</u>
- Boron has three valence electrons. Introducing Boron in Si will crate holes because the Boron takes one electron from Si to form covalent bonds in the Si lattice. Hence Boson is an <u>Acceptor.</u>





### **Doped Semiconductors (VII)**

- The donor electrons occupy energy states just below the conductivity band
- The holes created by the acceptors occupy energy states which are just above the zone with the bounded electrons.



30



### **Doped Semiconductors (VIII)**

- The carriers created via implant of impurities are called majority carriers. In general carriers can always be created via thermal excitation. Therefore there are always also minority carriers.
- In a p-type semiconductor the majority carriers are the holes and the minority carriers are the electrons.
- In an n-type semiconductor the majority carriers are electrons and the minority carriers are holes
- Electron and hole densities obey :

N-type	P-type
n <sub>n0</sub> =N <sub>D</sub>	p <sub>p0</sub> =N <sub>A</sub>
$n_{n0} p_{n0} = n_i^2$	$n_{p0} p_{p0} = n_i^2$
$\mathbf{p}_{\mathrm{n0}} = \mathbf{n}_{\mathrm{i}}^{2}/\mathrm{N}_{\mathrm{D}}$	$n_{p0} = n_i^2 / N_A$

#### Notation:

 $n_{n0}/p_{n0}$  = number of electrons/holes in n-type Semiconductor at thermal equilibrium  $N_{D}$  = number of donors

 $n_{p0}/p_{p0}$  = number of electrons/holes in p-type Semiconductor at thermal equilibrium

 $N_A$  = number of acceptors

2/18/2004

# pn-junction in open circuit (VII)

- As discussed before n-type of carriers will diffuse towards p-type and p-type of carriers will diffuse towards n-type creating I<sub>D</sub>. There they will recombine. This will leave '+' charges in the n-region and '-' charges in the p-region mostly close to the junction.
- Therefore a carrier-depleted region is created close to the junction.
- This charge creates a field that eventually stops the process.
- In addition minority carriers (thermally excited holes from n-type region or electrons from the p-type region) will through the depletion region. This will crate I<sub>s</sub> (drift current).
- Since no net current is flowing through the diode we have : I<sub>D</sub> = I<sub>S</sub>

• The Junction potential is given by:





# Depletion Region Depth (VIII)

- The charges from both sides of the depletion region are equal. Therefore:  $qx_pAN_A = qx_nAN_D \Rightarrow x_n/x_p = N_A/N_D$  where  $x_p$ ,  $x_n$  are the depths of each side of the depletion region and A is the area.
- The depletion region total depth is simply W<sub>dep</sub>=x<sub>p</sub>+ x<sub>n</sub>:

$$W_{dep} = [(2\epsilon_s/q)(1/N_A + 1/N_D)V_0]^{1/2}$$

<u>For Silicon:</u> ε<sub>s</sub>= 1.04 10<sup>-12</sup> F/cm W = 0.1 –1.0 μm



# pn-junction in reverse bias (IX)

- In reverse bias the n-side of the junction is connected to the '+' and the p-side to the '-' of a source.
- The external field has the same direction with the depletion region field resulting to a stronger field in the depletion region.
- The depletion region grows as more holes are transported to the n-side and more electrons in the p-side

Rm: 508, x47590

No current flows except of a small leakage current....

2/18/2004



Rm: 508, x47590

**The Depletion Capacitance (XI)**  

$$C_{j} = \frac{A \varepsilon_{s}}{\sqrt{\frac{2}{\varepsilon_{s}}} (\frac{1}{M_{s}} + \frac{1}{M_{b}})(V_{b} + V_{R})}} \xrightarrow{(3)}$$

$$C_{j} = \frac{A \varepsilon_{s}}{\sqrt{V_{b}(1 + \frac{V_{R}}{V_{b}})}} \xrightarrow{(3)} \sqrt{\frac{2}{\varepsilon_{s}}} (\frac{1}{M_{s}} + \frac{1}{M_{b}})}$$

$$C_{j} = \frac{A \varepsilon_{s}}{\sqrt{1 + \frac{V_{R}}{V_{b}}}} \xrightarrow{(A + \frac{V_{s}}{V_{s}})} \xrightarrow$$



#### The Diode in Forward Bias XII

- Majority carriers are supplied on both sides.
- They neutralize some of the uncovered bound charge.
- The <u>depletion layer narrows and the</u> <u>depletion voltage reduces</u>
- The diffusion current grows
- $\bullet \qquad \qquad \mathbf{I} = \mathbf{I}_{\mathbf{D}} \mathbf{I}_{\mathbf{S}}$



#### The Diode in Forward Bias XIII

#### The Saturation current can then be calculated



#### **Diffusion** Capacitance



**Diode display a capacitance** also in forward bias. Results to a *transit time*  $\tau_{\tau}$ 

2

 $\mathcal{Z} = \frac{L_p^2}{D_p} \implies Q_p = \mathcal{T}_p I_p$ IN GENERAL: Q = ZpIp+ZnIn or one an write Q = ZT.I TT = TRANSIT TIME Costas Foudas, Imperial College,

In most devices one of the sides is more heavily depped e.g  $N_A >> N \rightarrow I = I_p$  $C_1 = \frac{dQ}{dV} = \frac{Z_T}{V} I$ 

in practice 
$$C_j = \mathcal{L}C_{J_o}$$

2/18/2004

Rm: 508, x47590



#### Appendix II: Number of Carriers in Semiconductors

 Fermi Statistics is used to calculate the number of electron and hole carriers in a semiconductor.
 The explicit calculation is shown





#### Appendix II: Number of Carriers in a Semiconductor



2/18/2004



#### Appendix II: II





#### Appendix II: III



Costas Foudas, Imperial College, Rm: 508, x47590

2/18/2004

